

# Marking Scheme

1.

| Question |     |                       | Marking details  | Marks |
|----------|-----|-----------------------|--|-------|
| 3.       | (a) | (i)                   | $P = I^2R \quad 18 = I^2 \times 8 \text{ (1-sub), } I^2 = \frac{18}{8} \text{ (1-manip),}$<br>$I = 1.5 \text{ [A] (1-answer)}$<br><b>Award 2 marks for an answer of 2.25 [A]</b><br><b>Award 1 mark if substitution precedes manipulation.</b>   | 3     |
|          |     | (ii)                  | 3 [A] ecf - answer must be double the answer to (i)  | 1     |
|          |     | (iii)                 | Either $V = IR \quad V = 1.5 \text{ (ecf)} \times 8 \text{ (1-sub), } = 12 \text{ [V] (1)}$<br><b>ecf must be 8 × answer to (i)</b><br>Or accept $P = VI$ so $V = \frac{18}{1.5} \text{ (ecf) (1-sub+manip) } = 12 \text{ [V] (1)}$<br><b>ecf applies to 1.5 the value used must be the answer to (i)</b>  | 2     |
|          | (b) | (i)                   | <b>Either: <u>Supply</u> voltage is unchanged / current (don't accept amps) has decreased (1) so the circuit resistance must have increased. (1) The 2<sup>nd</sup> mark must be linked to the 1<sup>st</sup> mark.</b><br><br><b>OR voltage <u>across each bulb</u> has decreased (1) and so the current (don't accept amps) has decreased / but the resistance of each bulb has not changed (1) The 2<sup>nd</sup> mark must be linked to the 1<sup>st</sup> mark.</b> | 2     |
|          |     | (ii)                  | $P = I^2R = 0.75^2 \times 8 \text{ (1 - sub) } = 4.5 \text{ [W] (1)}$<br><b>Or accept <math>P = VI = 6 \text{ (ecf from (a)(iii)) } \times 0.75 \text{ (1 - sub) } = 4.5 \text{ [W] (1)}</math></b><br><b>Or accept <math>P = V^2 / R = 6^2 \text{ (ecf from (a)(iii)) } / 8 \text{ (1 - sub) } = 4.5 \text{ [W] (1)}</math></b>   | 2     |
|          |     | (iii)                 | Lamps are more powerful (brighter) [in parallel] / if one fails then the others will still work / they can be switched independently<br><b>Accept they have the <u>supply</u> voltage across them</b>  | 1     |
|          |     | <b>Question total</b> |  |       |

2.

| Question              |     | Marking details   | Mark       |
|-----------------------|-----|---|------------|
| 5.                    | (a) | Subs+manip 40/230 (1) $I = 0.17[4]$ [A] (1)<br>[Do not accept 0.173 but accept 0.2]   | 2          |
|                       | (b) | (i) Subs+manip $I^2 = \frac{118}{82}$ (1) = 1.44 (1), $I = 1.2$ [A] (1) If 1.44 on the answer line then award 2 marks. If 1.43 used, no penalty for rounding $I$ will = 1.19 [A] N.B. $\sqrt{1.4} = 1.18$<br><br>(ii) current through each lamp = $\frac{1.2(ecf)}{12} = 0.1$ [A] (1)<br><br><b>Either</b><br>pd across dimmer = $1.2 \times 82 = 98[.4]$ (1)<br>pd across lamps = $230 - 98.4$ ecf = 131.6 (accept 132)<br>power = $131.6$ ecf $\times 0.1$ ecf = 13.16 [W] (accept 13.2) (1)<br><br><b>OR</b> resistance of each lamp = $\frac{230}{0.174} = 1322$ (1) ecf for 0.174<br>Power = $0.1^2$ ecf $\times 1322$ ecf = 13.22 [W] (1) | 3          |
| <b>Question total</b> |     |   | <b>[8]</b> |


3.

| Question              |     |  | Answer / Explanatory Notes   | Marks Available |
|-----------------------|-----|--|--|-----------------|
| 1.                    | (a) | (i)  | 2 [A]  | 1               |
|                       |     | (ii)   | $R = \frac{6}{2}$ (1 –substitution) = 3 [Ω] (1) ecf from (i)<br>(If found for wire in (i) $R = 4.8 \Omega$ ) | 2               |
|                       |     | (iii)  | 3.25 [A]   | 1               |
|                       | (b) | (i)  | <b>Lamp</b> has bigger resistance or converse argument or values given $W = 4.8 \Omega$ and $L = 5.2 \Omega$ | 1               |
|                       |     | (ii)   | Smaller current through it or converse argument or calculations shown (allow temperature increase)           | 1               |
|                       | (c) | Beyond about 11 V, W has the bigger current (1) hence W has the bigger power (1)<br><b>Or power calculations</b> at 12 V (1) this is because the current in W is now bigger than in L (1)<br><b>Or</b> at 11 V the powers are equal (1) because the currents are equal (1) |  | 2               |
| <b>Question total</b> |     |  | <b>[8]</b>   |                 |

4.

| Question |     |      | Marking details  | Marks       |
|----------|-----|------|--|-------------|
| 4.       | (a) | (i)  | Voltmeter drawn with correct symbol in parallel with the lamp (allow a line through the voltmeter and allow other voltmeters across other components) (1)<br>Ammeter drawn with correct symbol in series with the resistor (1)<br>The [variable] resistor is altered / changes the resistance / resistor changes the current / resistor changes the voltage (1)<br>Take readings <u>each time</u> (1). | 4           |
|          |     | (ii) | Any diagonally upwards straight line from origin [as for a resistor] (1)<br>Diagonal line of correct gradient from origin award 2 marks.<br>Calculation of $I = 3$ A (at foot of page) (1)<br>Point (12, 3) plotted (1)<br>(Point at (12, 3) implies 2 <sup>nd</sup> mark so can be awarded).  | 3           |
|          | (b) | (i)  | $P = IV$ or $P = I^2R$ (1) or implied with correct substitution<br>Substitution (1)<br>Answer = 20.25 [W] (1) to be taken from their graph<br>Expected values are: 9 V ( $\pm 0.2$ ), $I = 2.25$ A ( $\pm 0.1$ )   | 3           |
|          |     | (ii) | Lamp has greater resistance (1) because it has the smaller current through it / allow calculations of 5.1 $\Omega$ [and 4 $\Omega$ ] (1) Accept converse argument for resistor. (Any reference to power treat as being neutral.)   | 2           |
|          |     |      | <b>Question total</b>  | <b>[12]</b> |

5.

| Question |     |      | Marking details  | Marks Available         |
|----------|-----|------|--|-------------------------|
| 1        | (a) | (i)  | Horizontal velocity = $\frac{1.20}{0.60} = 2[.0 \text{ m s}^{-1}]$   | 1                       |
|          |     | (ii) | $0 = u^2 - 2 \times 9.81 \times 0.44$ [correct substitution into $v^2 = u^2 + 2ax$ ] (1)<br>$u = 2.94 \text{ [m s}^{-1}]$ (1)<br><b>or</b><br>$0 = u - 9.81 \times 0.30$ [correct substitution into $v = u + at$ ] (1)<br>$u = 2.94 \text{ [m s}^{-1}]$ (1)<br><b>[Other solutions possible]</b> | 2                       |
|          | (b) | (i)  | $R = (4 + 8.64)^{1/2}$ (1) [ecf from (a)(i) and/or (a)(ii)]<br>$R = 3.56 \text{ [m s}^{-1}]$ (1)   | 2                       |
|          |     | (ii) | $\theta = 55.8^\circ$ ecf  | 1                       |
|          | (c) | (i)  | <u>Force of gravity on earth due to grasshopper</u>  | 1                       |
|          |     | (ii) | $F = 3 \times 10^{-5} \times 9.81 = 2.9 \times 10^{-4} \text{ [N]}$ Accept 0.3 m[N]  | 1                       |
|          | (d) |      |   | 1                       |
|          |     |      |  | <b>Question 1 Total</b> |