

1.


4. (a) Define the *potential difference* between two points in an electric circuit. [2]

.....

.....

.....

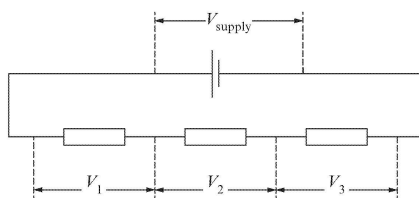- (b) Three resistors are connected as shown.




- (i) Complete the equation that relates **all** of the potential differences in the circuit: [1]

$V_{\text{supply}} = \dots\dots\dots$

- (ii) The equation you wrote down in (b)(i) is an example of which conservation law?[1]

.....

(c)

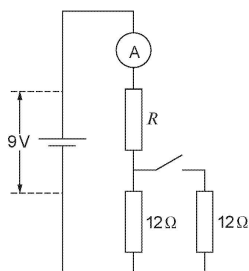

- (i) In the circuit shown, with the **switch open**, the ammeter reads 0.5 A. Show that  $R = 6\Omega$ . [2]

.....

.....

.....

- (ii) The switch is now **closed**.

- (i) Calculate the (new) potential difference across  $R$ . [2]

.....

.....

.....

- (ii) Calculate the (new) current through the ammeter. [2]

.....

.....

- (iii) More  $12\Omega$  resistors can be connected in parallel with the  $12\Omega$  resistors. Determine the **total** number of  $12\Omega$  resistors needed for the current through the ammeter to be 1.2 A. [4]

.....

.....

.....

.....

**2.**

- (a) Derive, giving a labelled diagram, the relationship between the current  $I$  through a metal wire of cross sectional area  $A$ , the drift velocity,  $v$ , of the free electrons, each of charge  $e$ , and the number,  $n$ , of free electrons per unit volume of the metal. [4]  
( $I = nAve$ ).

.....

.....

.....

.....

.....

- (b) Calculate the drift velocity of free electrons in a copper wire of cross sectional area  $1.7 \times 10^{-6} \text{ m}^2$  when a current of 2.0 A flows. [ $n_{\text{copper}} = 1.0 \times 10^{29} \text{ m}^{-3}$ ]. [2]

.....

.....

.....

- (c) A potential difference is required across the copper wire in order for the current to flow. The size of the current depends on the wire's *resistance*. Explain in terms of free electrons, how this resistance arises. [2]

.....

.....

.....

.....

- (d) The copper wire in (b) is of length 2.5 m. When it carries a current of 2.0 A, it dissipates energy at the rate of 0.1 W. Calculate its resistivity. [4]

.....

.....

.....

.....

.....

.....

.....


.....

- (e) A second copper wire has the same volume as the wire in (d), but is longer. Complete the table below indicating whether the quantity given is **bigger**, **smaller** or the **same** for this longer wire. [3]

Quantity	For the longer wire this quantity is ...
Cross-sectional Area	
$n$ , number of free electrons/unit volume	
Resistivity	

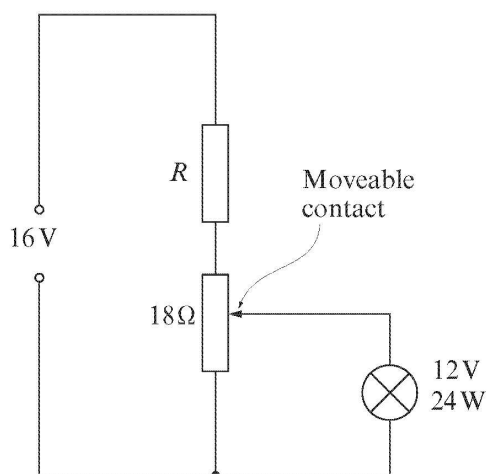3.

A student uses the circuit below to produce a current-voltage graph for a 12 V, 24 W filament lamp.




(a) Show clearly on the diagram the correct positions for the voltmeter and ammeter. [2]

(b) When the lamp is working normally, calculate

(i) the current flowing through it; [1]


(ii) its resistance. [1]

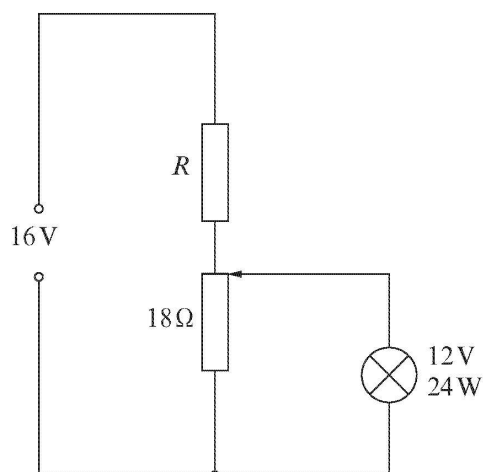(c) The value of  $R$  is chosen so that the voltage across the lamp can be varied between 0 V and 12 V. The circuit below shows the position of the moveable contact when the lamp is operating normally (i.e. at 12 V).



Calculate the required value of  $R$ . [4]

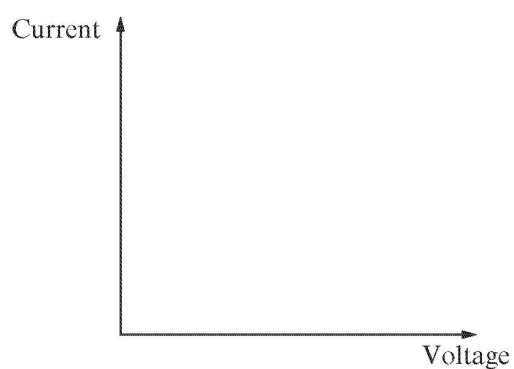(d) Sketch on the axes below the current-voltage graph expected for the filament lamp. [2]



4. (a) (i) State Ohm's law. [2]

.....


.....

.....

- (ii) What can be said about the resistance of a conductor that obeys Ohm's law? [1]

.....

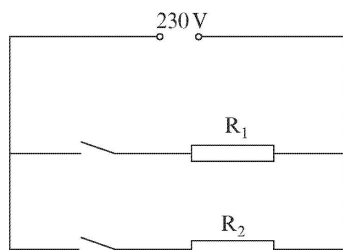- (b) The heating circuit of a hairdryer consists of two heating elements  $R_1$  and  $R_2$  connected in parallel as shown. The elements are made from wire of the same material of resistivity  $95 \times 10^{-8} \Omega \text{m}$  and diameter  $1.4 \times 10^{-4} \text{m}$ .



- (i) The length of wire used to make  $R_1$  is 3.2m. Show that the resistance of  $R_1$  is approximately  $200 \Omega$ . [3]

.....

.....

.....

- (ii) Calculate the power output from the heating circuit with only  $R_1$  switched on. [1]

.....

.....

- (iii) With both elements switched on the **total resistance** is only a third of the resistance of  $R_1$  on its own. Calculate the resistance of  $R_2$ . [3]

.....

.....

.....

.....

.....

- (iv) Explain which element,  $R_1$  or  $R_2$ , would provide the greater power output from the heating circuit. [2]

.....

.....

.....


- (v) Calculate the total current with both elements switched on. [1]

.....

.....

**5.**

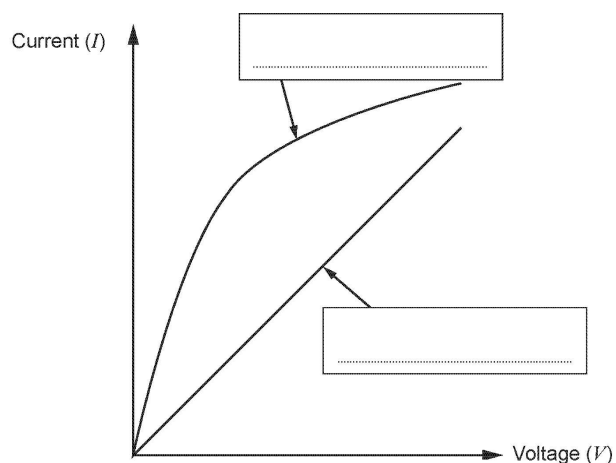- (a) Graphs are drawn for a metal wire at constant temperature and for the filament of a lamp.



- (i) Complete the boxes, labelling the graphs with the component they represent. [1]
- (ii) Suggest reasons for the different shapes of the two graphs. [5]

[illegible]


(b) X and Y are two lamps.

- (i) Lamp X is labelled at 12 V, 24 W. Calculate the current in the lamp when it operates at its rated voltage. [1]

.....

.....

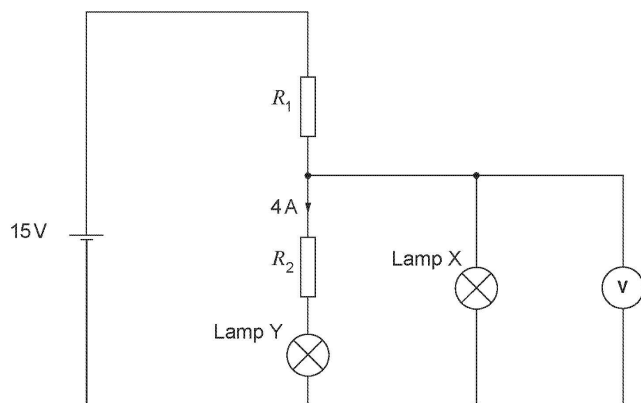- (ii) Lamp Y is labelled at 6 V, 4 A. In the following circuit, the values of  $R_1$  and  $R_2$  are chosen so that **both lamps operate at their rated voltages**.



- (I) State the reading on the voltmeter. .... [1]

- (II) Calculate the pd across  $R_2$ . [1]

.....

- (III) Calculate  $R_2$ . [1]

.....

- (IV) Calculate  $R_1$ . [3]

.....

.....

.....

.....

.....